

Digital Electronics and Microprocessor Systems (ELEC211)

Dave McIntosh and Valerio Selis

dmc@liv.ac.uk

v.selis@liv.ac.uk

Digital 1: Basic gates and function implementation


Dave McIntosh
Room 508, EEE building
Office hour: Wednesday at 2 pm (email first)

Outline


- Digital electronics in context
- Logic gates (revision)
- Combinational logic (revision)
- Karnaugh maps (revision)
- Minterms and maxterms (revision)
- Implementing functions (revision)

<https://www.youtube.com/watch?v=Fxv3JoS1uY8>

 Course textbook – please borrow and use it!



Digital electronics in context

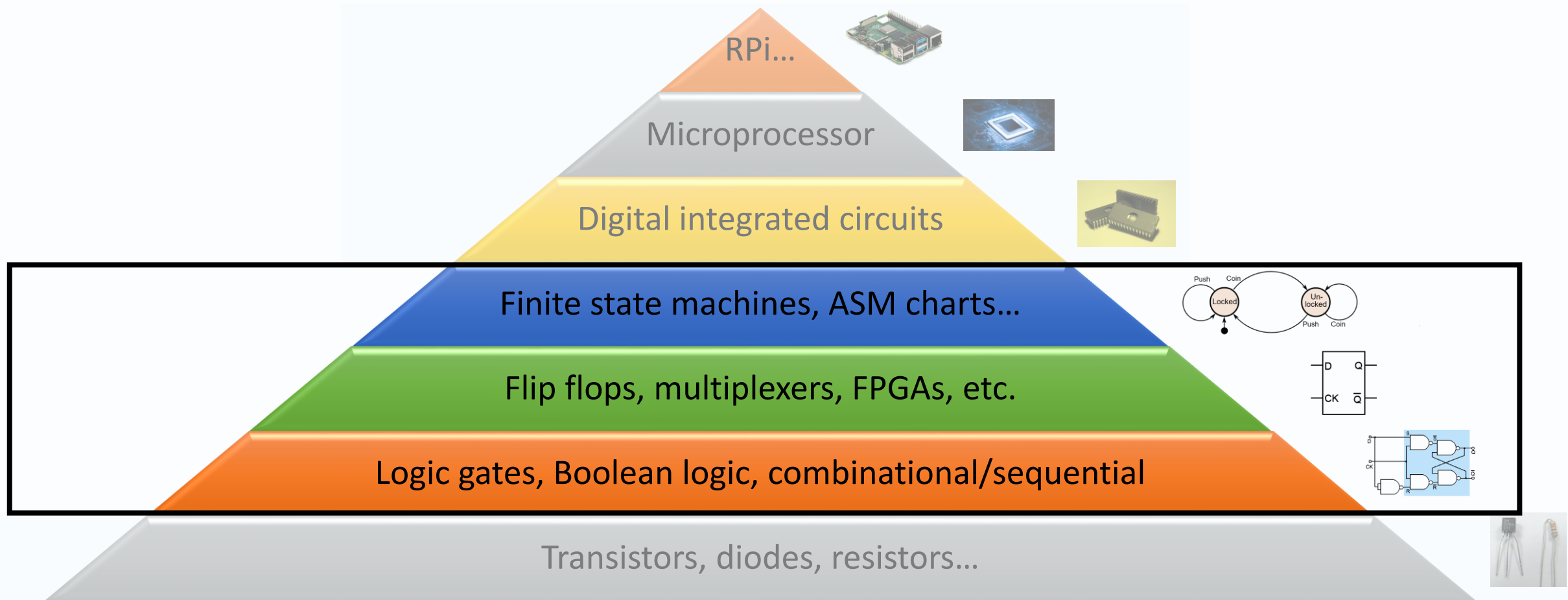


Logic gates: basic operations (revision)


Logic gates use Boolean algebra

Basic operations are:


NOT

 

AND

 


OR

 

The NOT gate or inverter

The circuit symbol is

 

The **truth table** is


A	X
0	1
1	0

The notation is

$$X = \bar{A}$$

$$X = A'$$

AND

 


$$X = A \cdot B$$

$$X = A \wedge B$$

<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	0
1	0	0
1	1	1

OR

 


$$X = A + B$$

$$X = A \vee B$$

<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	1

XOR

 


Exclusive OR

$$X = A \oplus B$$


<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0

3+ inputs?

NOT?

 


AND

 

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$X = A \cdot B \cdot C$$


OR

 

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$X = A + B + C$$

XOR ...?


 


A	B	C	X	Rarely seen
0	0	0	0	
0	0	1	1	
0	1	0	1	
0	1	1	0	This interpretation: "one and only one"
1	0	0	1	
1	0	1	0	Alternative: "odd parity"
1	1	0	0	
1	1	1	0	

$$X = A \oplus B \oplus C$$

Inverted versions of these gates...


“Buffer”

  

A	X
0	0
1	1

$$X = A$$


NAND

 

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$X = \overline{A \cdot B \cdot C}$$


NOR

 

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$X = \overline{A + B + C}$$


XNOR (2 input)

 

A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

$$X = \overline{A \oplus B}$$

XNOR

 


Exclusive NOR

$$X = \overline{A \oplus B}$$

<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	1

XOR

 

Exclusive OR

$$X = A \oplus B$$

<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0

Notations

AND

$$A.B \quad (A \wedge B)$$

OR

$$A + B \quad (A \vee B)$$

Inversion
("complementation")


$$\overline{X} \quad (X')$$

Universal gates

NAND and NOR are 'universal gates'

Each one can implement any Boolean function without using other gates...

e.g. NAND as NOT

 

- NAND and NOR gates are cheaper to produce than other gates
- NAND gates are routinely used to build the other gates in circuits
- Particularly if buying in bulk, many NAND gates may be bought instead of purchasing all types



Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?



$$X = (\overline{A \cdot B}) \cdot (A + B)$$



Groups of 2 or 3

1. Draw circuit diagram

2. Use the individual truth tables to construct a combined truth table



Combinational and sequential circuits

- **Combinational circuits:**
 - Output depends only on **present input** (easier)
- **Sequential circuits:**
 - Output values depend on **present *and* past** values
 - Circuit 'remembers' its own **state**
- **Combinational logic** uses **Boolean algebra**.

Laws of Boolean Algebra

Operations with 0	$X+0=X$	$X \cdot 0=0$
Operations with 1	$X+1=1$	$X \cdot 1=X$
Idempotent laws	$X+X=X$	$X \cdot X=X$
Involution law	$(X')'=X$	
Laws of complementarity	$X+X'=1$	$X \cdot X'=0$
Commutative laws	$X+Y=Y+X$	$X \cdot Y=Y \cdot X$
Associative laws	$(X+Y)+Z=X+(Y+Z)=X+Y+Z$	$(XY)Z=X(YZ)=XYZ$
Distributive laws	$X(Y+Z)=XY+XZ$	$X+YZ=(X+Y)(X+Z)$

Laws / theorems of Boolean Algebra

Simplification theorem (1)	$X \cdot Y + X \cdot Y' = X$	$(X + Y) \cdot (X + Y') = X$
Simplification theorem (2)	$X + X \cdot Y = X$	$X \cdot (X + Y) = X$
Simplification theorem (3)	$(X + Y') \cdot Y = X \cdot Y$	$X \cdot Y' + Y = X + Y$
DeMorgan's laws	$(X + Y + Z + \dots)' = X' \cdot Y' \cdot Z' \dots$	$(X \cdot Y \cdot Z \dots)' = X' + Y' + Z' \dots$
Multiplying and factoring	$(X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$	$X \cdot Y + X' \cdot Z = (X + Z) \cdot (X' + Y)$
Consensus theorem	$X \cdot Y + Y \cdot Z + X' \cdot Z = X \cdot Y + X' \cdot Z$	$(X + Y) \cdot (Y + Z) \cdot (X' + Z) = (X + Y) \cdot (X' + Z)$

BUT KARNAUGH MAPS ARE USUALLY MORE EFFICIENT THAN SIMPLIFYING ALGEBRAICALLY!

(To be continued....)

Minterms

A	B	C	Minterms	Maxterms
0	0	0	$A'B'C'=m_0$	$A+B+C=M_0$
0	0	1	$A'B'C=m_1$	$A+B+C'=M_1$
0	1	0	$A'BC'=m_2$	$A+B'+C=M_2$
0	1	1	$A'BC=m_3$	$A+B'+C'=M_3$
1	0	0	$AB'C'=m_4$	$A'+B+C=M_4$
1	0	1	$AB'C=m_5$	$A'+B+C'=M_5$
1	1	0	$ABC'=m_6$	$A'+B'+C=M_6$
1	1	1	$ABC=m_7$	$A'+B'+C'=M_7$

Minterm: a product term which outputs a logic high for one combination of A, B and C and their inverses.

Example:

For the combination **A=1, B=0, C=1**, the only product term worth 1 is $A.B'C$.

*[Let $A = 1, B = 0, C = 1$, then:
 $A.B'C = 1.1.1 = 1$]*

The binary number 101 is 5 as a decimal, so we call this minterm 5, m_5

Maxterms

A	B	C	Minterms	Maxterms
0	0	0	$A'B'C'=m_0$	$A+B+C=M_0$
0	0	1	$A'B'C=m_1$	$A+B+C'=M_1$
0	1	0	$A'BC'=m_2$	$A+B'+C=M_2$
0	1	1	$A'BC=m_3$	$A+B'+C'=M_3$
1	0	0	$AB'C'=m_4$	$A'+B+C=M_4$
1	0	1	$AB'C=m_5$	$A'+B+C'=M_5$
1	1	0	$ABC'=m_6$	$A'+B'+C=M_6$
1	1	1	$ABC=m_7$	$A'+B'+C'=M_7$

Maxterm: a sum term which outputs a logic LOW for one combination of A, B and C and their inverses.

Example:

For the combination **A=1, B=0, C=1**, the only sum term worth 0 is $A' + B + C'$.

[Let $A = 1, B = 0, C = 1$, then:
 $A' + B + C' = 0 + 0 + 0 = 0$]

The binary number 101 is 5 as a decimal, so we call this maxterm 5, M_5

Implement a function using minterms & maxterms

Consider the function, f , represented by this truth table.

We only want f to take a logic 'high' value for the combinations of A , B , C in the final five rows ($ABC = 011, 100, 101, 110, 111$).

How can we implement this using logic gates?

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Minterms and the Sum of Products

We can derive an expression for the output, f , by ORing together the product terms that make $f = 1$ for the desired combinations:

$$f = (A'BC) + (AB'C') + (AB'C) + (ABC') + (ABC)$$

This is called a SUM OF PRODUCTS (SOP)

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Maxterms and the Product of Sums

We can also write f by ANDing together the product terms that make $f = 0$ for the desired combinations:

$$f = (A+B+C)(A+B+C')(A+B'+C)$$

This is called a **PRODUCT OF SUMS (POS)**

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Minimum SOP

Before implementing using logic gates, it makes sense to minimise (simplify) the sum of products expression using Boolean laws:

$$f = (A'BC) + (AB'C') + (AB'C) + (ABC') + (ABC)$$

$$= A'BC + A(B'C' + B'C + BC' + BC)$$
$$= A'BC + A(B'(C' + C) + B(C' + C))$$
$$= A'BC + A(B' + B) = BC + A$$

The above expression is simplified using:

- 1st: Distributive law (factored out)
- 2nd: Complement law (C' + C = 1)
- 3rd: Identity law (A + 0 = A)
- 4th: Associative law (A + (B + C) = (A + B) + C)
- 5th: Absorption theorem (A + AB = A)

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


What is a simpler way to minimise this?

Minimum SOP and implementation

<i>A</i>	<i>B</i>	<i>C</i>	<i>f</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$f = (A' \cdot B \cdot C) + (A \cdot B' \cdot C') + (A \cdot B' \cdot C) + (A \cdot B \cdot C') + (A \cdot B \cdot C)$$

<i>f</i>	<i>A'B'</i>	<i>A'B</i>	<i>AB</i>	<i>AB'</i>
<i>C'</i>			1	1
<i>C</i>		1	1	1

 


Maxterms – minimum POS

- As noted, we can also write f by ANDing together the combinations of values that make it 0 (maxterms):

$$f = (A+B+C)(A+B+C')(A+B'+C)$$

C \ AB				
	00	01	11	10
0	0	0	1	1
1	0	1	1	1

$$f = BC + A$$

 

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Combinational logic: minterms

Combinational logic expressions can be expressed as a sum of minterms ('canonical sum of products') as follows:

$$f(C,B,A) = m_2 + m_5 + m_7$$

$$f(C,B,A) = \sum m(2,5,7)$$

m_2 , m_5 and m_7 are minterms; we can substitute them in:

$$m_2 = C'BA' \quad m_5 = CB'A \quad m_7 = CBA$$

$$f = C'BA' + CB'A + CBA = C'BA' + CA$$

Minterms & Maxterms

<i>A</i>	<i>B</i>	<i>C</i>	Minterms	Maxterms
0	0	0	$A'B'C'=m_0$	$A+B+C=M_0$
0	0	1	$A'B'C=m_1$	$A+B+C'=M_1$
0	1	0	$A'BC'=m_2$	$A+B'+C=M_2$
0	1	1	$A'BC=m_3$	$A+B'+C'=M_3$
1	0	0	$AB'C'=m_4$	$A'+B+C=M_4$
1	0	1	$AB'C=m_5$	$A'+B+C'=M_5$
1	1	0	$ABC'=m_6$	$A'+B'+C=M_6$
1	1	1	$ABC=m_7$	$A'+B'+C'=M_7$

Sum of Products (SOP)

Product of Sums (POS)

$$m_2 + m_5 + m_7 = \Sigma m(2,5,7)$$

$$M_2 \cdot M_5 \cdot M_7 = \Pi M(2,5,7)$$

$$A'BC' + AB'C + ABC = A'BC' + AC$$

$$(A + B' + C)(A' + B + C')(A' + B' + C')$$





Question



- Substitute in the minterms to give the following ‘canonical sum of products’ as a sum of product terms, and simplify (if possible).

$$f(C,B,A) = \sum m(0,3,6)$$




Question

- By substituting in the minterms and simplifying, rewrite the following 'canonical sum of products' expression as a minimum sum of products (minimum SOP).

$$f(D, C, B, A) = \sum m(1, 4, 8, 9, 14)$$

Summary and suggested reading

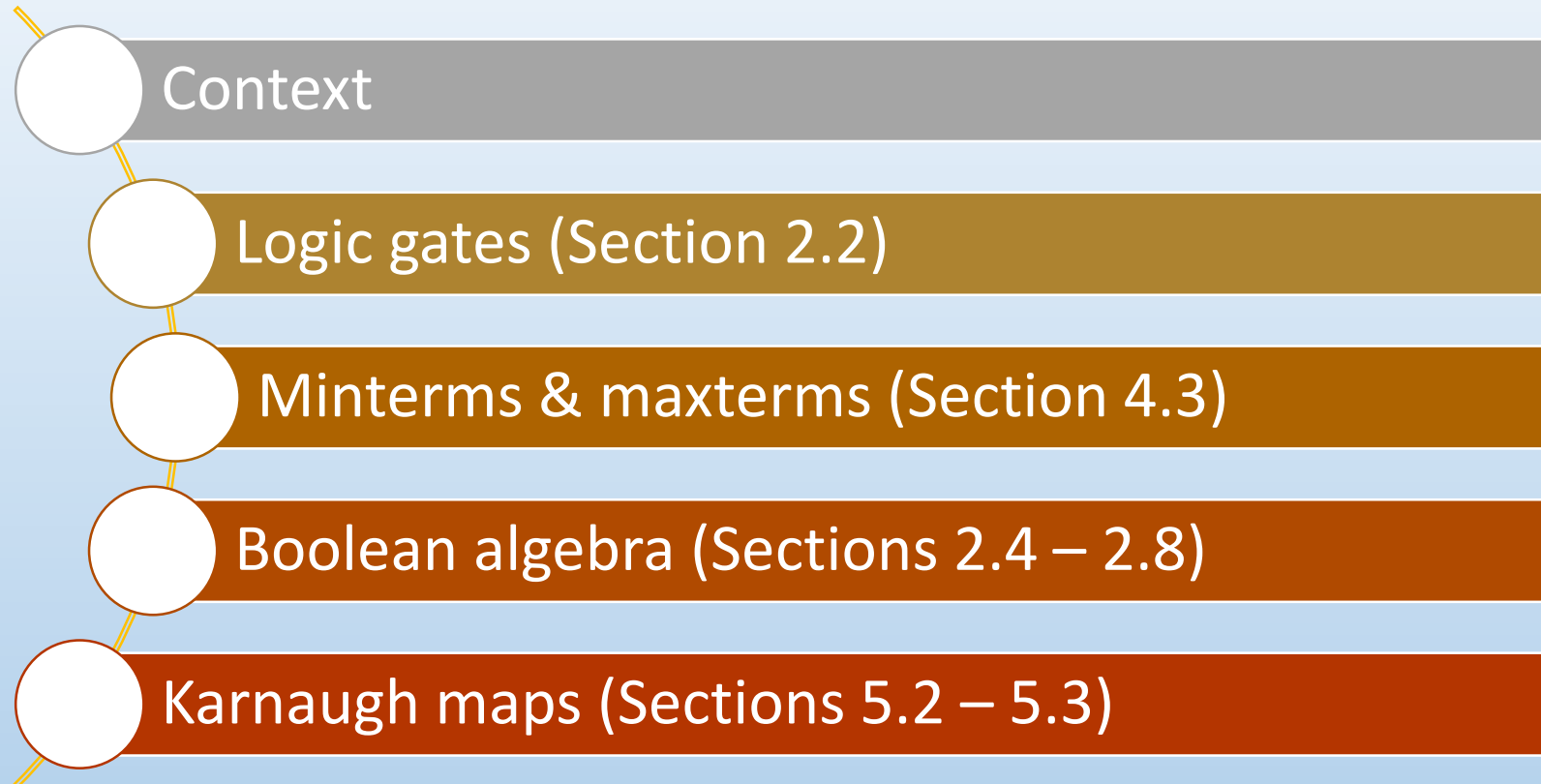

Next lecture is this
Wednesday at 12.00
in the **Chadwick**
Barkla lecture
theatre:
Multiplexers,
decoders, encoders...

Roth and Kinney *Fundamentals of Logic Design*

