

# Digital Electronics and Microprocessor Systems (ELEC211)

**Dave McIntosh** and Valerio Selis

[dmc@liv.ac.uk](mailto:dmc@liv.ac.uk)

[v.selis@liv.ac.uk](mailto:v.selis@liv.ac.uk)

Week 7 Q&A

# Week 7 – Lecture 17

## Digital Electronics


### Introduction to sequential logic


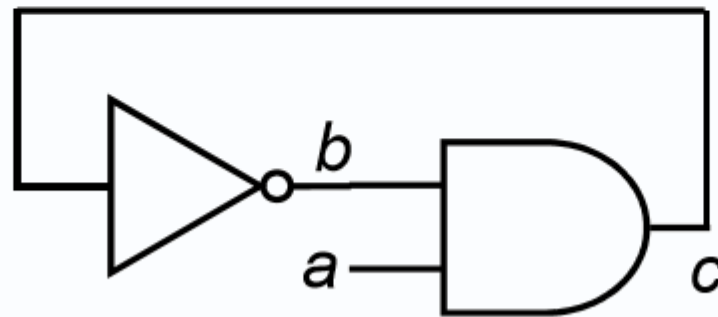
# Question





The inverter in the figure has a propagation delay of 4 ns and the AND gate of 8 ns. Draw a timing diagram for the circuit showing a, b, c. a and c are initially equal to 0, b is initially one. After 20 ns a becomes 1 for 90 ns and then 0 again.


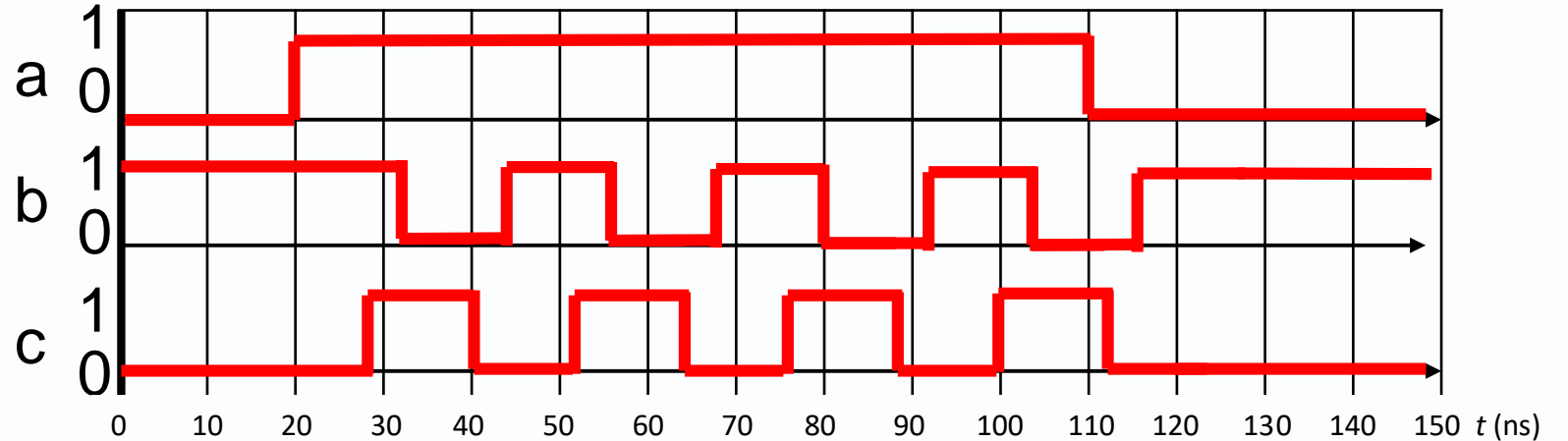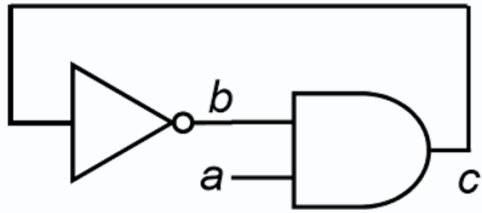
# Answer

The inverter in the figure has a propagation delay of 4 ns and the AND gate of 8 ns. Draw a timing diagram for the circuit showing a, b, c. a and c are initially equal to 0, b is initially one. After 20 ns a becomes 1 for 90 ns and then 0 again.



# Week 7 – Lecture 18

## Digital Electronics

**CPLDs & FPGAs**

**Shannon's expansion**



# Question

## Shannon's expansion (decomposition)



Decompose the following function into 2 functions, one for  $a'$  and the other for  $a$ .

$$\begin{aligned} f(a, b, c, d) &= a'c'd' + abd + bcd + b'cd' + acd' \\ &= a'f_0 + af_1 \end{aligned}$$

*(4 to 3 variable example)*



# Method

$$f(a,b,c,d) = a'c'd' + abd + bcd + b'cd' + acd'$$

$$= a'c'd' + abd + (a + a')bcd + (a + a')b'cd' + acd'$$

$ab \backslash cd$					
		00	01	11	10
00					
01					
11					
10					

$f$

$ab \backslash cd$		$a=0$		$a=1$	
		00	01	11	10
00					
01					
11					
10					

$f_0 \quad f_1$

*(4 to 3 variable example)*

$$= a'(\dots) + a(\dots)$$

# Answer

$$f(a,b,c,d) = a'c'd' + abd + bcd + b'cd' + acd'$$

$$= a'c'd' + abd + (a + a')bcd + (a + a')b'cd' + acd'$$

$ab \backslash cd$	00	01	11	10
00	1	1	0	0
01	0	0	1	0
11	0	1	1	0
10	1	0	1	1

$f$

$ab \backslash cd$	$a=0$		$a=1$	
	00	01	11	10
00	1	1	0	0
01	0	0	1	0
11	0	1	1	0
10	1	0	1	1

$f_0$        $f_1$

(4 to 3 variable example)

$$f = a'(c'd' + b'd' + bcd) + a(cd' + bd) \quad (\text{answer})$$





# Question



Decompose the following function into 2 functions, one for  $a'$  and the other for  $a$ .

$$\begin{aligned} f(a, b, c, d, e) &= b'c'd' + a'be + b'cde' + ab'd' + bcde \\ &= a'f_0 + af_1 \end{aligned}$$

*(5 to 4 variable example)*



# Method

$$f(a,b,c,d,e) = b'c'd' + a'be + b'cde' + ab'd' + bcde$$

$$= (a + a')b'c'd' + a'be' + (a + a')cde' + ab'd' + (a + a')bcde$$

$a=0$

$bc \backslash de$	00	01	11	10
00				
01				
11				
10				

$bc \backslash de$	00	01	11	10
00				
01				
11				
10				

$a=1$

**(5 to 4 variable example)**

$$= a'(\dots) + a(\dots)$$

# Answer

$$f(a,b,c,d,e) = b'c'd' + a'be + b'cde' + ab'd' + bcde$$

$$= (a + a')b'c'd' + a'be' + (a + a')cde' + ab'd' + (a + a')bcde$$

		<i>bc</i>			
		00	01	11	10
<i>de</i>	00	1	0	0	0
	01	1	0	1	1
	11	0	0	1	1
	10	0	1	0	0

$a=0$

		<i>bc</i>			
		00	01	11	10
<i>de</i>	00	1	1	0	0
	01	1	1	0	0
	11	0	0	1	0
	10	0	1	0	0

$a=1$

*(5 to 4 variable example)*



$$f = a'(b'c'd' + be + b'cde') + a(b'd' + b'ce' + bcde) \text{ (answer)}$$